

# Electricity

4. a. Ideal conductors have no resistance and are thus labelled as wires.

b. Assuming  $R_{\text{copper}} \ll R_{\text{bulb}}$ ,  $\frac{V^2}{R} = P$

$$I = \frac{P}{V} = \frac{10}{12} = 0.83 \text{ A} \quad (2 \text{ sf}) \quad \Rightarrow R = \frac{V^2}{P} = 14.4 \Omega$$

c. Assumptions:

①:  $R_{\text{copper}} \ll R_{\text{bulb}}$

$$\rho_{\text{copper}} \sim 10^{-8} \Omega \text{ m} \Rightarrow R_{\text{copper}} \sim \frac{10^{-8}}{10^{-6}} = 10^{-2} \Omega$$

So, this is a justified assumption.

②: (as 12 V is the terminal PD, internal resistance doesn't matter)

d.  $V_b = 12 \text{ V}$ ,  $R_b = 0.03 \Omega$

e. The bulb is now modelled as a wire

f.  $I = \frac{V_b}{R_b} = 400 \text{ A}$

If left connected, the high output power will drain the battery quickly.



g.  $V(t) = 5 \sin(2000\pi t)$

h.  $r = 10\ \Omega, R = 100\ \Omega$

$$I = \frac{V_s}{R+r} \quad V_t = \frac{V_s R}{R+r} = \frac{50}{11} \sin(2000\pi t)$$

i.  $4.9 = 5 \cdot \frac{R}{R+r}$

$$\Rightarrow 4.9R + 4.9r = 5R$$

$$\Rightarrow 0.1R = 4.9r$$

$$\Rightarrow r = R = \frac{1}{5} \cdot \frac{1}{4.9} R = 2.0\ \Omega \text{ (2sf)}$$

5 a.  $R_{AB} = \frac{1}{\frac{1}{3} + \frac{1}{6}} + \frac{1}{\frac{1}{3} + \frac{1}{6}} = 4\ \Omega$

b.  $V_{eff} = 90\text{V}, R_{eff} = 30\ \Omega$   
 $I = 3\text{A}$

c. Unless the sequence  $R_1, R_2, R_3, \dots$  (term) fits tests for convergence,  $R \rightarrow \infty$

d. Unless  $\frac{1}{R_1} + \frac{1}{R_2} \dots$  converges to a finite value,  $R \rightarrow \infty$



d. First condition,  $I_1 = I_2 = I$ ,  $I R_1 = 5V$ ,  $I R_2 \neq 0V$   
 $\Rightarrow R_2 = 2R_1$

second:  $I_2 = I_1 - I_3$   $I_3 = 1mA$

$I_1 R_1 = 7V$   $I_1 R_2 - I_3 R_2 = 8V$

$\Rightarrow I_1 R_1 - I_3 R_1 = 4V$

$\Rightarrow I_3 R_1 = 3V \Rightarrow R_1 = \frac{3}{1 \times 10^{-3}} = 3k\Omega$

$R_2 = 6k\Omega$

6 a.  $C_{eq} = \frac{1}{\frac{1}{2.2} + \frac{1}{1.68}} = 0.95 \mu F (2sf)$

b.  $V_R = IR$ ,  $V_C = \frac{Q}{C} = \frac{\int i dt}{C}$ ,  $V_L = L \frac{di}{dt}$

c. Resistor;  ~~$i(t) = V(t)$~~   $i(t) = \frac{V(t)}{R}$

Capacitor,  $i(t) = +C \omega V_0 \cos(\omega t)$

inductor;  $i(t) = -\frac{V_0}{\omega L} \cos(\omega t)$

d.  $P_R(t) = \frac{V_0^2}{R} \cos^2(\omega t)$   $P_C = C \omega V_0^2 \sin \omega t \cos \omega t$

e.  $\langle P_R \rangle = \frac{V_0^2}{2R}$ ,  $\langle P_L \rangle = \langle P_C \rangle = 0$   $P_L = \frac{V_0^2}{\omega L} \sin \omega t \cos \omega t$